

# Linear Microwave Circuits: From $\vec{a}$ to $Z_o$

## Outline

- Phasors
- Impedance
- Transmission Lines
- Wave Representation
- Scattering Matrices
- Smith Charts
- Johnson Noise
- Noise Wave Correlation Matrices
- Supermix **sdata** class
- Linear Connection Theory
- Subnet Growth in Supermix

# Phasors

- Work in **frequency space**
- Sinusoids have **magnitude** and **phase**
- Complex number have magnitude and phase

We can represent  $V$  and  $I$  as complex numbers

$$V(\omega, t) = \text{Re}[V\sqrt{2} e^{j\omega t}]$$

$$I(\omega, t) = \text{Re}[I\sqrt{2} e^{j\omega t}]$$

$Z$  may also be complex to show the relative phase between  $V$  and  $I$


$$V = I Z$$

# Capacitance

$$Q = CV$$

$$\frac{dQ}{dt} = C \frac{dV}{dt}$$

$$I = C \frac{dV}{dt}$$

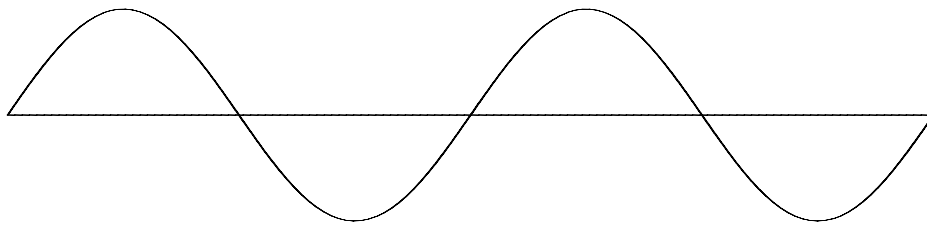

$$V = V_o e^{j\omega t}$$


$$I = j\omega CV$$

$$Z = \frac{-j}{\omega C}$$

Current **LEADS** voltage by  $\frac{\pi}{2}$

# Inductance

$$V = L \frac{dI}{dt}$$

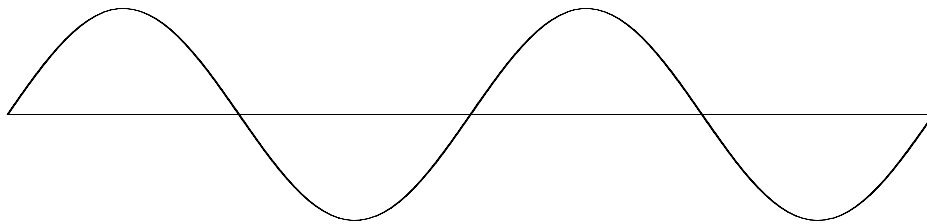

$$V = V_o e^{j\omega t}$$


$$V_o e^{j\omega t} dt = L dI$$

$$\frac{1}{j\omega} V = LI$$

$$Z = j\omega L$$

Current **LAGS** voltage by  $\frac{\pi}{2}$

# Transmission Lines

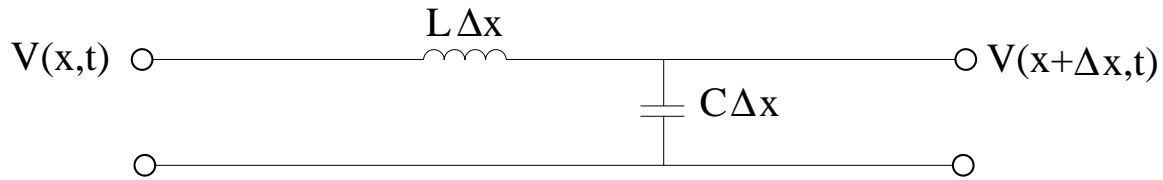

Kirchhoff's Laws give

$$V(x + \Delta x, t) - V(x, t) = -L \Delta x \frac{\partial I}{\partial t}$$

$$I(x + \Delta x, t) - I(x, t) = -C \Delta x \frac{\partial V}{\partial t}$$

So

$$\frac{\partial V}{\partial x} = -L \frac{\partial I}{\partial t}$$

$$\frac{\partial I}{\partial x} = -C \frac{\partial V}{\partial t}$$

This is equivalent to the wave equations:

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^2 I}{\partial x^2} = LC \frac{\partial^2 I}{\partial t^2}$$

## Transmission Lines (Continued)

These give traveling wave solutions

$$V = V_o e^{j\omega(t - \sqrt{LC}x)}$$

$$I = I_o e^{j\omega(t - \sqrt{LC}x)}$$

The phase velocity is

$$c = \frac{1}{\sqrt{LC}}$$


We can find Z from Kirchhoff's Laws

$$\frac{\partial I}{\partial x} = -C \frac{\partial V}{\partial t}$$

$$-j\omega\sqrt{LC} I = -j\omega CV$$

$$Z_o = \sqrt{\frac{L}{C}}$$

# The Wave Representation

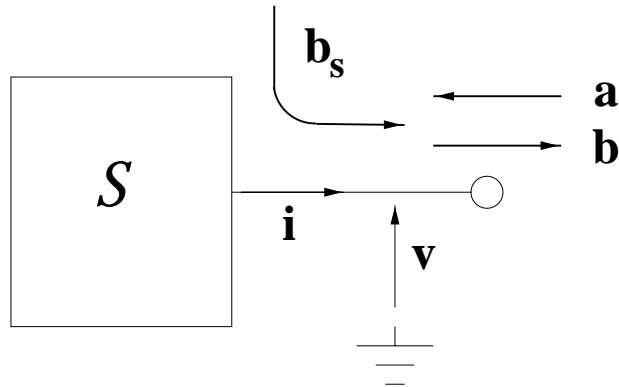

Incoming ( $\mathbf{a}$ ) and outgoing ( $\mathbf{b}$ ) waves are defined as

$$a_i = \frac{1}{2\sqrt{Z_0}} (V_i + Z_0 I_i) \quad \text{and} \quad b_i = \frac{1}{2\sqrt{Z_0}} (V_i - Z_0 I_i)$$

Power can be computed

$$P_i = |a_i|^2 - |b_i|^2 \quad \text{or} \quad P = \mathbf{a}^\dagger \mathbf{a} - \mathbf{b}^\dagger \mathbf{b}$$

The scattering matrix is defined by

$$\mathbf{b} = \mathcal{S} \mathbf{a} + \mathbf{b}_s$$

## $\mathcal{S}$ For Reciprocal Circuits

- Circuits are reciprocal if
  - Linear
  - Time invariant
  - Normal materials
  - No current or voltage sources
- Transmission is the same in both directions, so
$$S_{ij} = S_{ji}$$
- This tells us nothing about reflections ( $S_{11}$ ,  $S_{22}$ , etc.)



## $\mathcal{S}$ For Lossless Circuits

If a passive circuit has no loss, then

$$\mathbf{b}^\dagger \mathbf{b} = \mathbf{a}^\dagger \mathbf{a}$$

$$\mathbf{b} = \mathcal{S} \mathbf{a}$$

$$\mathbf{b}^\dagger = \mathbf{a}^\dagger \mathcal{S}^\dagger$$

$$\mathbf{a}^\dagger \mathcal{S}^\dagger \mathcal{S} \mathbf{a} = \mathbf{a}^\dagger \mathbf{a}$$

$$\mathcal{S}^\dagger \mathcal{S} = \mathcal{I}$$

$\Rightarrow \mathcal{S}$  is unitary

# Scattering Matrix Examples

- Ideal Transmission Line

$$\mathcal{S} = e^{-j\theta} \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix}$$

$$S_{12} = S_{21} \quad \Rightarrow \quad \text{Reciprocal}$$

$$\mathcal{S}^\dagger \mathcal{S} = \mathcal{I} \quad \Rightarrow \quad \text{Lossless}$$

- Series Resistor

$$r \equiv \frac{R}{Z_o} \quad \mathcal{S} = \frac{1}{2+r} \begin{pmatrix} r & 2 \\ 2 & r \end{pmatrix}$$

$$S_{12} = S_{21} \quad \Rightarrow \quad \text{Reciprocal}$$

$$\mathcal{S}^\dagger \mathcal{S} \neq \mathcal{I} \quad \Rightarrow \quad \text{Lossy}$$

- Amplifier


$$\mathcal{S} = \begin{pmatrix} 0 & 0 \\ 10 & 0 \end{pmatrix}$$

$$S_{12} \neq S_{21} \quad \Rightarrow \quad \text{Not Reciprocal}$$

$$\mathcal{S}^\dagger \mathcal{S} \neq \mathcal{I} \quad \Rightarrow \quad \text{Lossy}$$

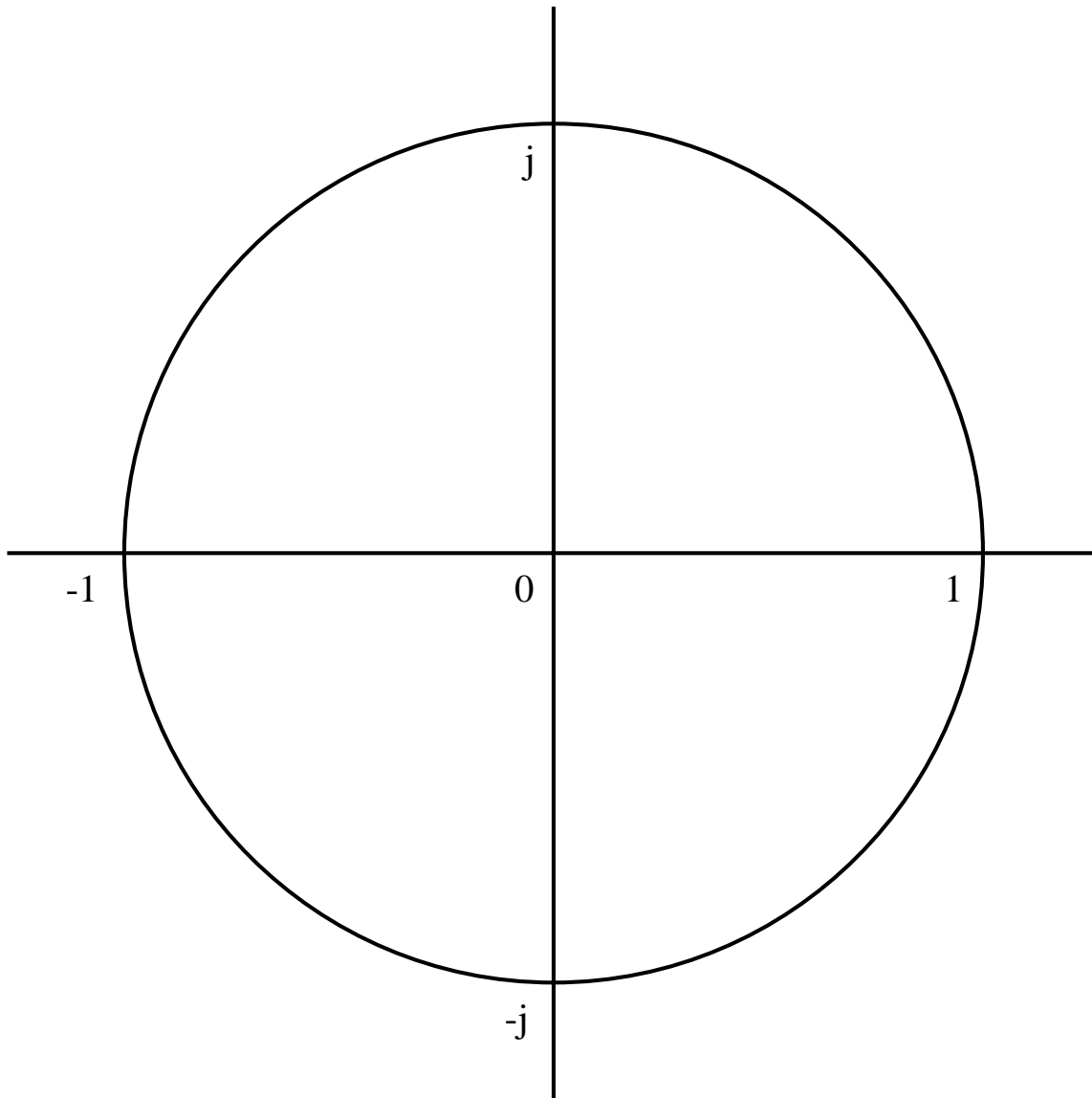
# Reflections

Polar plot of  $\Gamma = \frac{b_i}{a_i}$


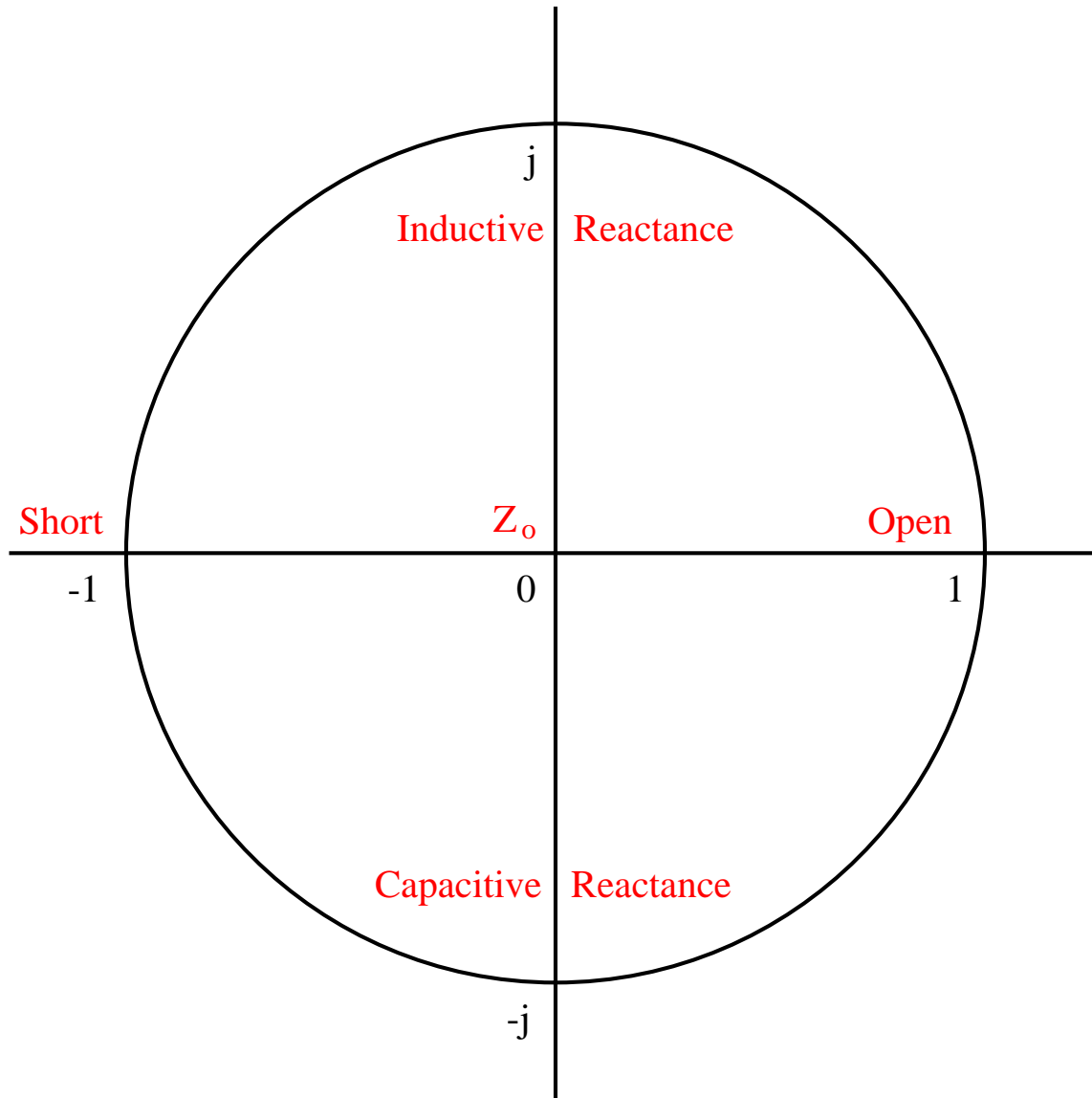
# Reflections

Polar plot of  $\Gamma = \frac{b_i}{a_i}$



# Johnson Noise

- Power generated by a resistor at temperature  $T$  is

$$P = k_B T \Delta f$$

- Rayleigh-Jeans Limit

$$f \ll \frac{k_B T}{h}$$

- Like a 1-d black body
- Only created in lossy circuits
- $R$  affects how the noise couples into the circuit

## Noise Waves

- Real devices generate noise

$$\mathbf{b} = \mathcal{S} \mathbf{a} + \mathbf{c}$$

- $\mathbf{c}$  is random, but we know the spectral density

$$\overline{|c_i|^2}$$


- Be careful adding noise waves

$$P = \overline{|c_1 + c_2|^2} = \overline{|c_1|^2} + \overline{|c_2|^2} + 2 \operatorname{Re}[\overline{c_1 c_2^*}]$$

- The noise wave correlation matrix is

$$\mathcal{C} \equiv \overline{\mathbf{c} \mathbf{c}^\dagger}$$

# Noise Waves

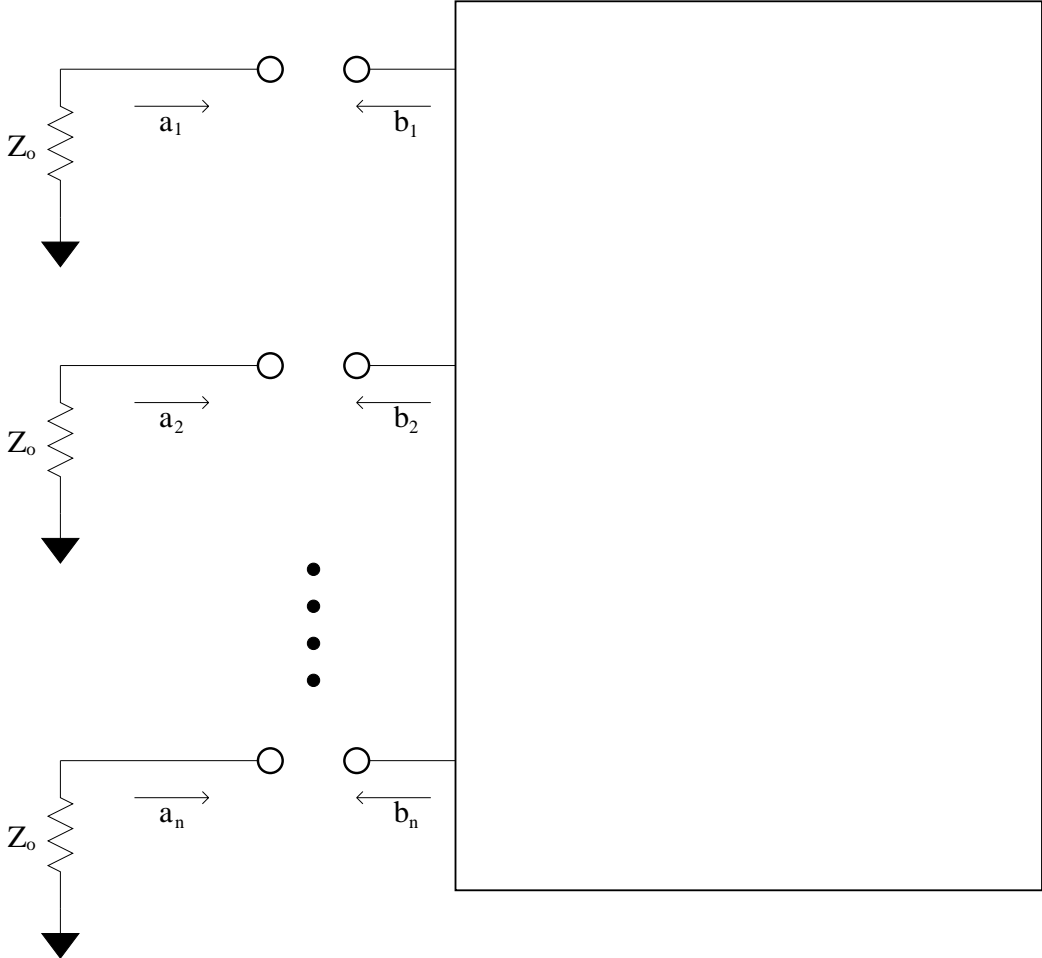

# Noise Matrix for Passive Circuits

- Have passive linear circuit with  $n$  ports
- Terminate each port with impedance  $Z = Z_o$
- Circuit is in thermal equilibrium at temperature  $T$
- Uncorrelated Johnson noise from the terminators, so

$$\overline{|a_i|^2} = k_B T$$

$$\overline{a_i a_j^*} = 0 \quad (i \neq j)$$

$$\overline{a a^\dagger} = k_B T \mathcal{I}$$

- Thermodynamic equilibrium requires

$$\overline{|b_i|^2} = \overline{|a_i|^2}$$

$$\overline{b_i b_j^*} = 0 \quad (i \neq j)$$

$$\overline{b b^\dagger} = k_B T \mathcal{I}$$

- Can now compute  $\mathcal{C}$  from the scattering relation

$$\mathbf{b} = \mathcal{S} \mathbf{a} + \mathbf{c}$$

$$\overline{\mathbf{b} \mathbf{b}^\dagger} = \mathcal{S} \overline{\mathbf{a} \mathbf{a}^\dagger} \mathcal{S}^\dagger + \overline{\mathbf{c} \mathbf{c}^\dagger}$$

$$k_B T \mathcal{I} = k_B T \mathcal{S} \mathcal{S}^\dagger + \mathcal{C}$$

$$\mathcal{C} = k_B T (\mathcal{I} - \mathcal{S} \mathcal{S}^\dagger)$$



# Noise in Passive Circuits


- Depends only on  $S$  and temperature

$$C = \frac{h\nu}{2} \coth\left(\frac{h\nu}{2k_B T}\right) (\mathcal{I} - SS^\dagger)$$

- Hyperbolic cotangent adds quantum noise for low  $T$ :

$$\frac{h\nu}{2} \coth\left(\frac{h\nu}{2k_B T}\right) \approx k_B T \quad \text{if } T \gg \frac{h\nu}{2k_B}$$
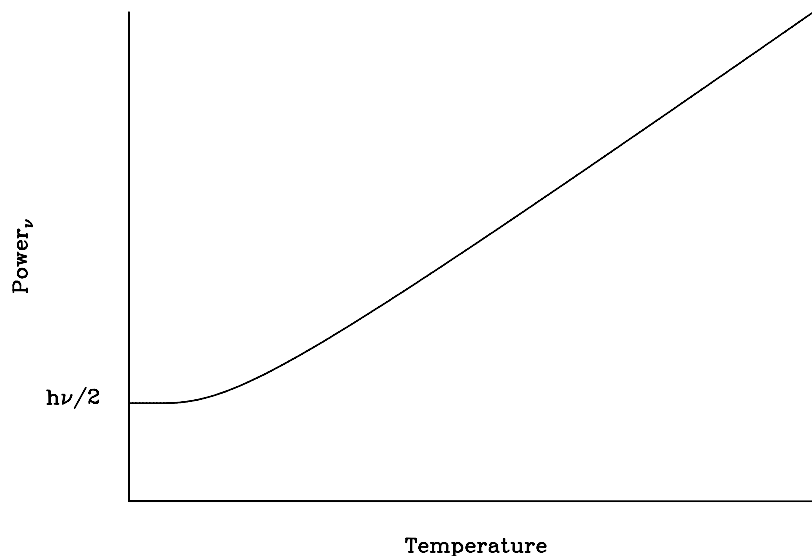
$$\frac{h\nu}{2} \coth\left(\frac{h\nu}{2k_B T}\right) \approx \frac{h\nu}{2} \quad \text{if } T \ll \frac{h\nu}{2k_B}$$



# Supermix sdata class

```
// *****
//
// class sdata
//
// sdata holds linear circuit data, including scattering
// matrix, noise correlation matrix, and source vector.
//
// *****
class sdata
{
protected:
    double z_norm;    // what characteristic impedance was used

public:
    Matrix S;    // scattering matrix
    Matrix C;    // noise correlation matrix
    Vector B;    // source vector, in square root of power

    int size() const;

    // convert sdata values to "engineering" forms:


    // Returns S parameter in dB for in -> out
    double SdB(int out, int in) const;

    // Returns noise temperature referred to input
    double tn(int out, int in) const;


    // Returns noise figure referred to input
    double NF(int out, int in) const;

    // Calculates noise matrix for a passive element using the
    // scattering matrix, temperature, and frequency.
    sdata & passive_noise(double freq, double temp) ;
};
```

# Connecting Linear Circuits

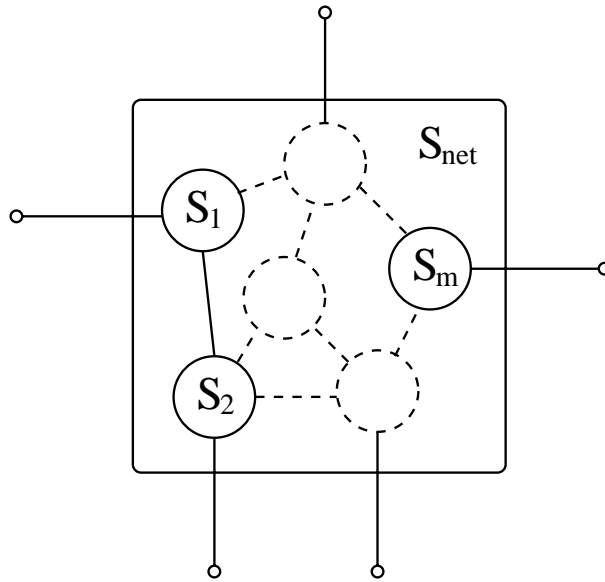
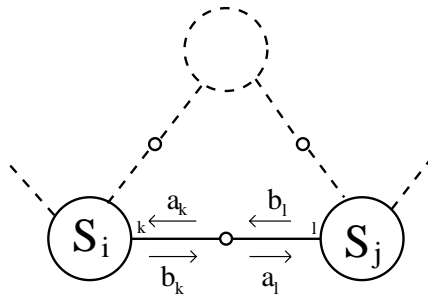
$$\begin{pmatrix} \mathbf{b}_1 \\ \mathbf{b}_2 \\ \vdots \\ \mathbf{b}_m \end{pmatrix} = \begin{pmatrix} S_1 & 0 & \dots & 0 \\ 0 & S_2 & \dots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \dots & S_m \end{pmatrix} \begin{pmatrix} \mathbf{a}_1 \\ \mathbf{a}_2 \\ \vdots \\ \mathbf{a}_m \end{pmatrix} + \begin{pmatrix} \mathbf{c}_1 \\ \mathbf{c}_2 \\ \vdots \\ \mathbf{c}_m \end{pmatrix}$$



$$\mathbf{b} = \Gamma \mathbf{a}$$

# $S$ Matrix for Connected Circuits

- Start with  $m$  independent scattering relations

$$\begin{pmatrix} \mathbf{b}_1 \\ \mathbf{b}_2 \\ \vdots \\ \mathbf{b}_m \end{pmatrix} = \begin{pmatrix} \mathcal{S}_1 & 0 & \dots & 0 \\ 0 & \mathcal{S}_2 & \dots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \dots & \mathcal{S}_m \end{pmatrix} \begin{pmatrix} \mathbf{a}_1 \\ \mathbf{a}_2 \\ \vdots \\ \mathbf{a}_m \end{pmatrix} + \begin{pmatrix} \mathbf{c}_1 \\ \mathbf{c}_2 \\ \vdots \\ \mathbf{c}_m \end{pmatrix}$$

- Rearrange to separate external and internal ports

$$\begin{pmatrix} \mathbf{b}_e \\ \mathbf{b}_i \end{pmatrix} = \begin{pmatrix} \mathcal{S}_{ee} & \mathcal{S}_{ei} \\ \mathcal{S}_{ie} & \mathcal{S}_{ii} \end{pmatrix} \begin{pmatrix} \mathbf{a}_e \\ \mathbf{a}_i \end{pmatrix} + \begin{pmatrix} \mathbf{c}_e \\ \mathbf{c}_i \end{pmatrix}$$

- Write port connections as a matrix relation

$$\mathbf{b}_i = \Gamma \mathbf{a}_i$$

- Write the desired (sourceless) scattering relation

$$\mathbf{b}_e = \mathcal{S}_{net} \mathbf{a}_e$$

- Solve for  $\mathcal{S}_{net}$

$$\mathcal{S}_{net} = \mathcal{S}_{ee} + \mathcal{S}_{ei}(\Gamma - \mathcal{S}_{ii})^{-1}\mathcal{S}_{ie}$$

# Noise Matrix for Connected Circuits

- Start as before, except  $\mathbf{a}_e = 0$  and  $\mathbf{c}_{\text{net}} = \mathbf{b}_e$

$$\begin{pmatrix} \mathbf{c}_{\text{net}} \\ \mathbf{b}_i \end{pmatrix} = \begin{pmatrix} \mathcal{S}_{ee} & \mathcal{S}_{ei} \\ \mathcal{S}_{ie} & \mathcal{S}_{ii} \end{pmatrix} \begin{pmatrix} \mathbf{0} \\ \mathbf{a}_i \end{pmatrix} + \begin{pmatrix} \mathbf{c}_e \\ \mathbf{c}_i \end{pmatrix}$$

- Write port connections as a matrix relation

$$\mathbf{b}_i = \Gamma \mathbf{a}_i$$

- Solve for  $\mathbf{c}_{\text{net}}$

$$\mathbf{c}_{\text{net}} = \mathcal{S}_{ei}(\Gamma - \mathcal{S}_{ii})^{-1} \mathbf{c}_i + \mathbf{c}_e$$


- Rearrange the input noise matrices to create  $\mathcal{C}_s$

$$\mathcal{C}_s \equiv \begin{pmatrix} \overline{\mathbf{c}_e \mathbf{c}_e^\dagger} & \overline{\mathbf{c}_e \mathbf{c}_i^\dagger} \\ \overline{\mathbf{c}_i \mathbf{c}_e^\dagger} & \overline{\mathbf{c}_i \mathbf{c}_i^\dagger} \end{pmatrix}$$


- Compute  $\mathcal{C}_{\text{net}} = \overline{\mathbf{c}_{\text{net}} \mathbf{c}_{\text{net}}^\dagger}$

$$\mathcal{C}_{\text{net}} = [\mathcal{I} | \mathcal{S}_{ei}(\Gamma - \mathcal{S}_{ii})^{-1}] \mathcal{C}_s [\mathcal{I} | \mathcal{S}_{ei}(\Gamma - \mathcal{S}_{ii})^{-1}]^\dagger$$

# Connection Types

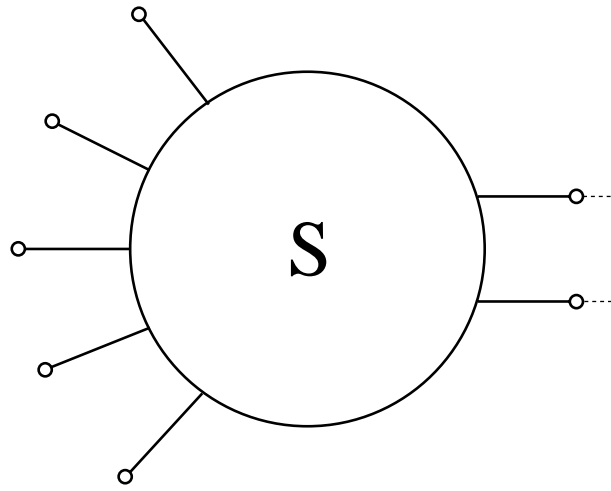

Intra-Connection

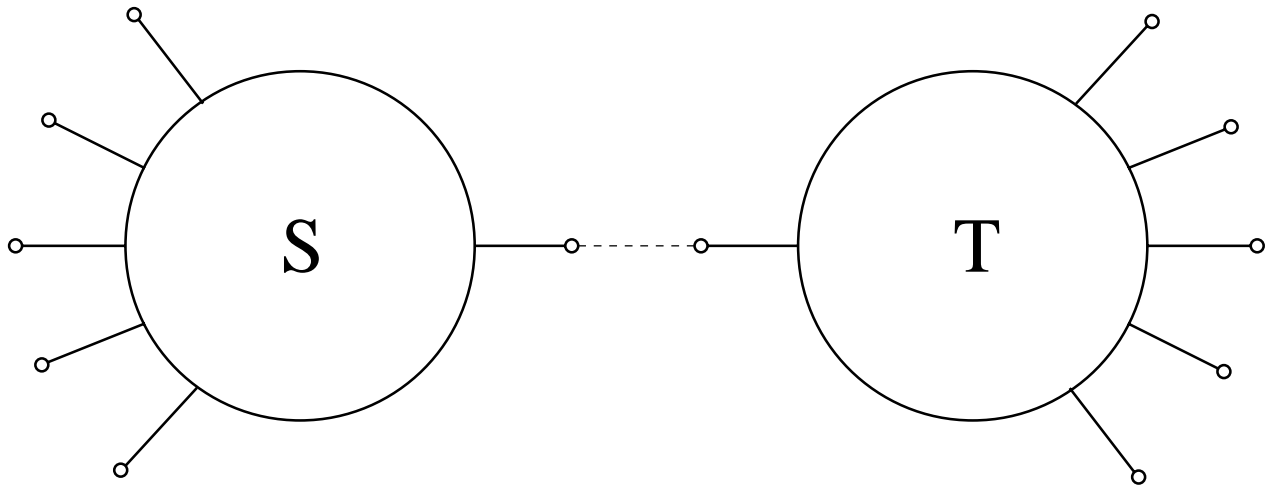

Inter-Connection

